

Solution to Assignment #2

Note: The solution provided here is just a design example to demonstrate the design process. There is no unique answer to this assignment.

To find the optimal biasing point, $V_{ds}=4V$ is selected as recommended by datasheet. V_{gs} should be selected based on the required I_{ds} which controls noise and gain performance. The transistor is a HEMT, which means the DC bias is negative. According to the data sheet (or DC simulation in ADS) the pinch-off voltage is $\sim -0.5V$, which means the gate has to be biased between $-0.5V$ and $0V$ for amplifier design. Figure 1 shows how to select V_{gs} for Cases I and II separately. According to the figure, $V_{gs}=-0.2V$ and $-0.3V$ are selected for Case 1 and 2, respectively. Figure 2(a) shows the schematic of the transistor, including the biasing and stability networks for Case II (Case I would be very similar). The transmission lines are 90° at the operating frequency. DC blocks are chosen to be $50pF$ which provide sufficiently small impedance at RF frequency (e.g., 1.5Ω at $2GHz$).



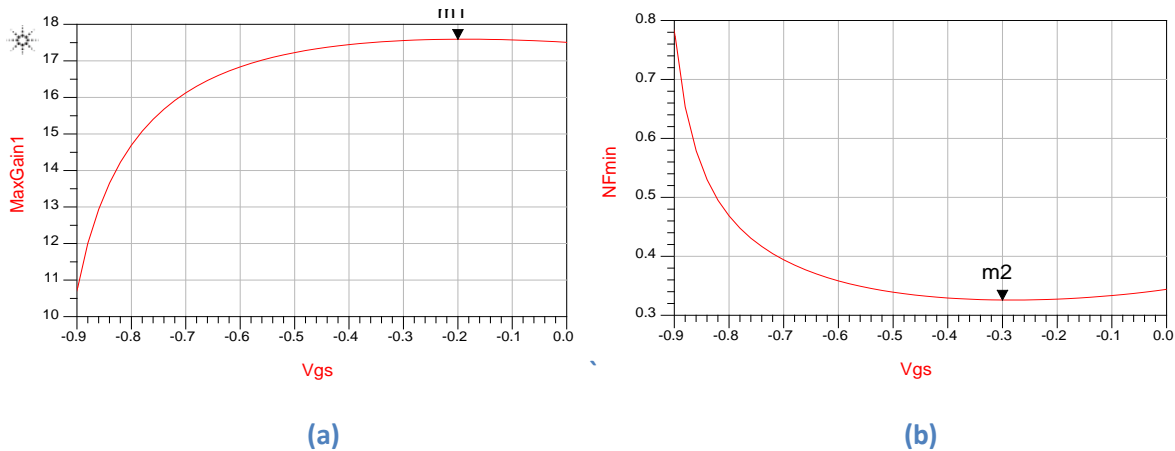


Figure 1. V_{gs} selection for (a) Case I, and (b) Case II

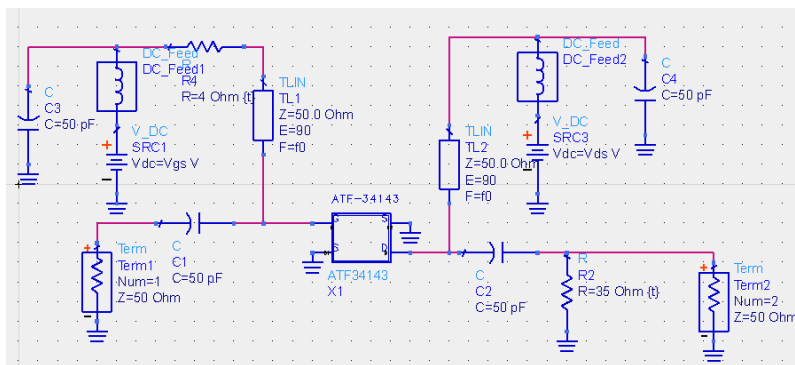

(a) Schematic

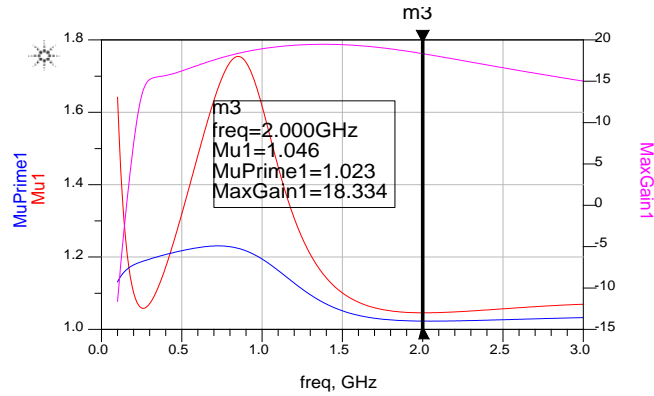

(b) Stability analysis

Figure 2. Case II biasing and stability circuitry

freq	MaxGain1	SmGamma1	SmGamma2
3.000 GHz	15.520	0.853 / 140.525	0.761 / 158.614

(a)

freq	MaxGain1	SmGamma1	SmGamma2
2.000 GHz	18.342	0.884 / 102.033	0.786 / 150.315

(b)

Figure 3. $G_{T_{\text{max}}}$, Γ_{MS} and Γ_{ML} for (a) Case I, and (b) Case II.**Design for Case I**

Step 1. Plot $G_A = G_{T_{\text{max}}} - 1\text{dB}$ circle as well as various constant-noise circles. Find the noise circle that is tangent to the G_A circle.

Step 2. Choose Γ_S as the intersection of the two circles. This ensures $G_A = G_{T_{\text{max}}} - 1\text{dB}$ while achieving the best possible NF. According to Figure 4,

$$\Gamma_S = 0.575 \angle 141.1^\circ$$

Step 3. Calculate $\Gamma_L = \Gamma_{\text{out}}^* = \left(S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1-S_{11}\Gamma_S} \right)^* = 0.590 \angle 165.8^\circ$

Step 4. Design input matching network from 50Ω to Γ_S or from Γ_S^* to 50Ω (why?).

Likewise, design output matching network from 50Ω to Γ_L or from Γ_L^* to 50Ω .

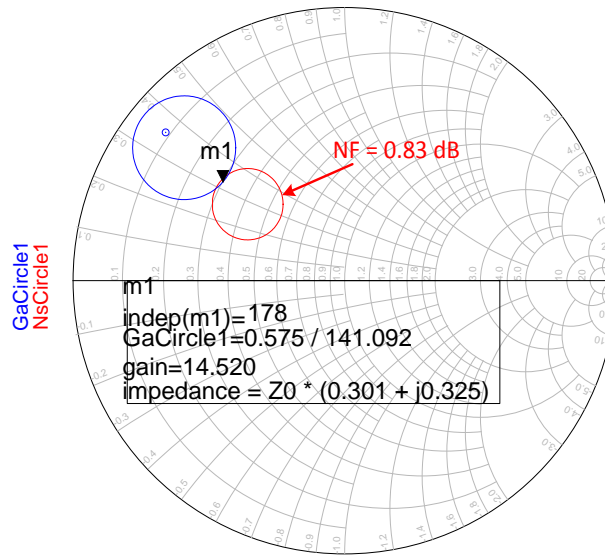


Figure 4

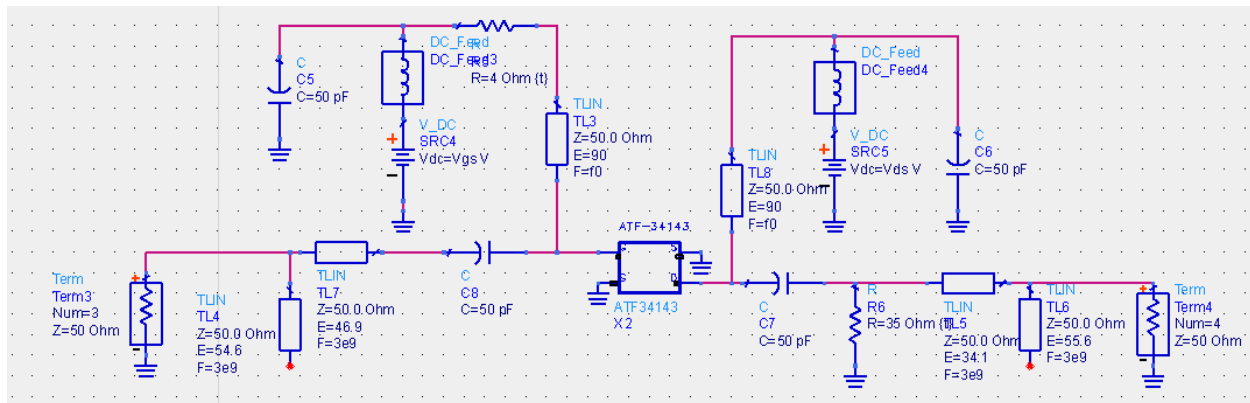


Figure 5

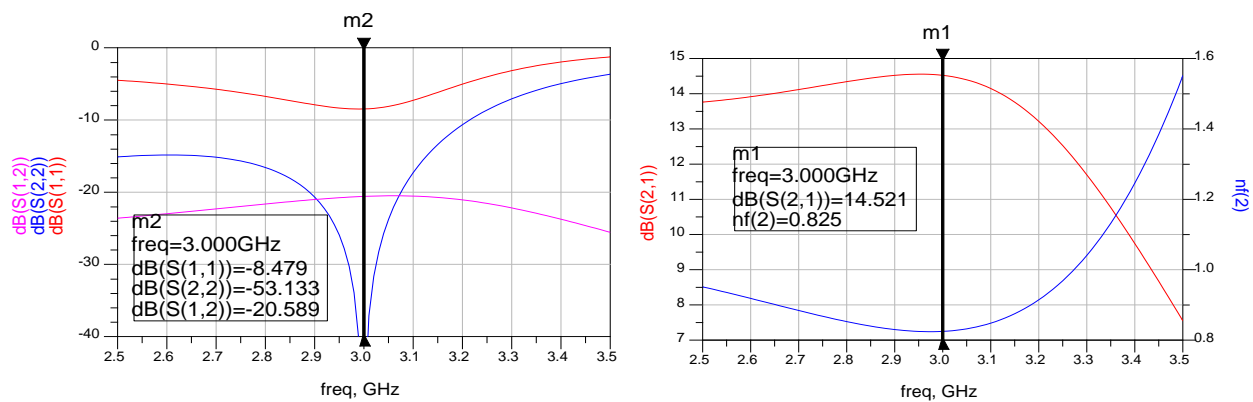


Figure 6

Design for Case II

Step 1. Plot $G_A = 16dB$ and $NF = 1dB$ circles.

Step 2. Choose Γ_S as the intersection of the two circles (or somewhere inside the overlapping area). This ensures $G_A > 16dB$ and $NF < 1dB$ (some margin has been considered to ensure the specifications are met). According to Figure 7,

$$\Gamma_S = 0.607 \angle 104.5^\circ$$

Step 3. Calculate $\Gamma_L = \Gamma_{out}^* = \left(S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1-S_{11}\Gamma_S} \right)^* = 0.578 \angle 157.5^\circ$

Step 4. Design input matching network from 50Ω to Γ_S or from Γ_S^* to 50Ω .

Likewise, design output matching network from 50Ω to Γ_L or from Γ_L^* to 50Ω .

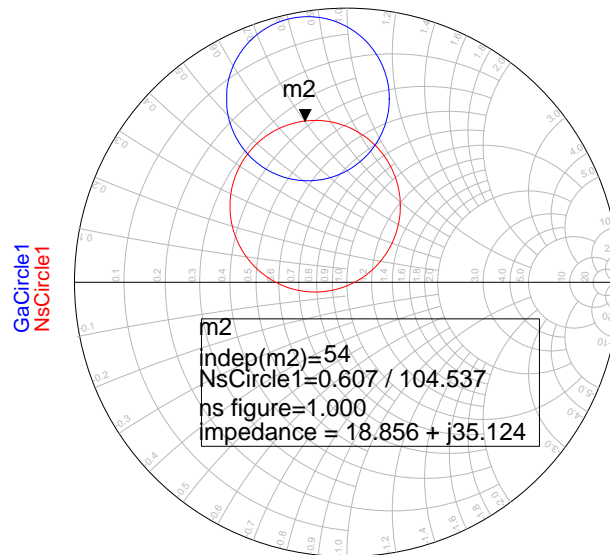


Figure 7

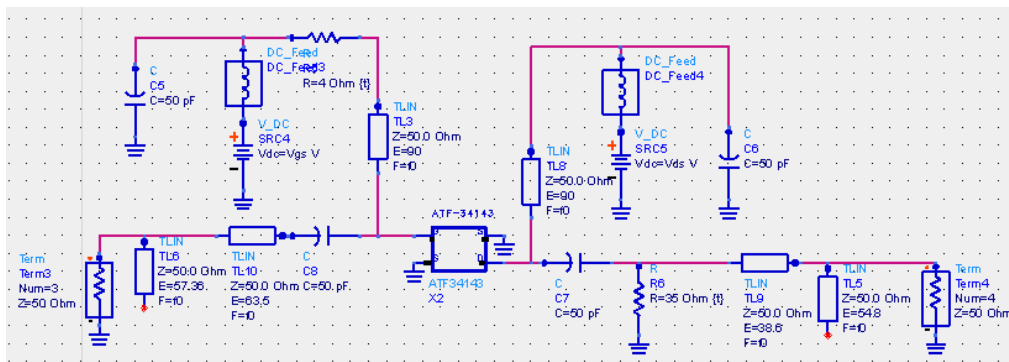


Figure 8

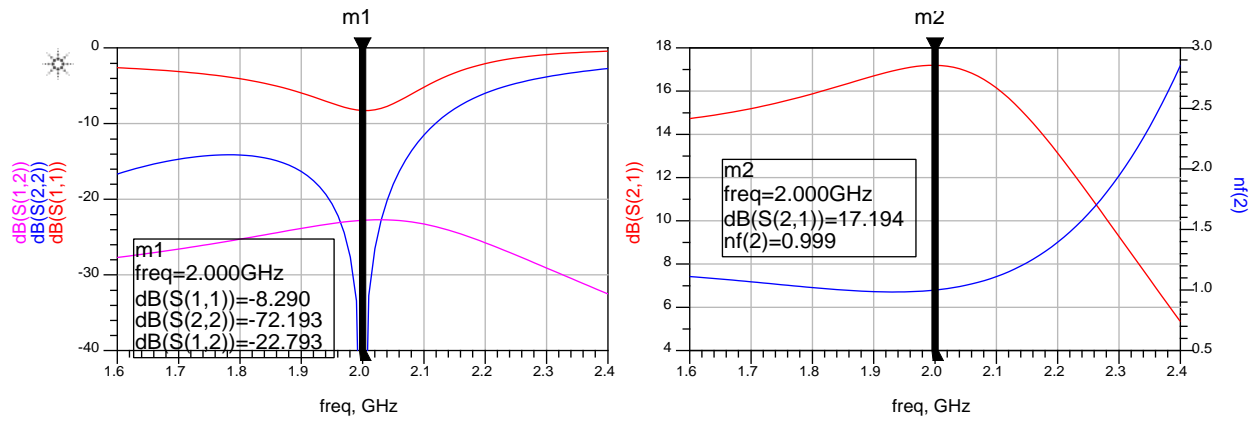


Figure 9