
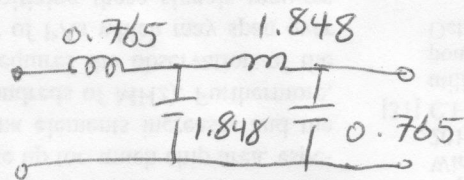


Q1) From Fig. 8.26 $\rightarrow N=4$ $\left| \frac{13.6}{8.0} \right| - 1 = 0.7$


From Table 8.3 \rightarrow LP Prototype:

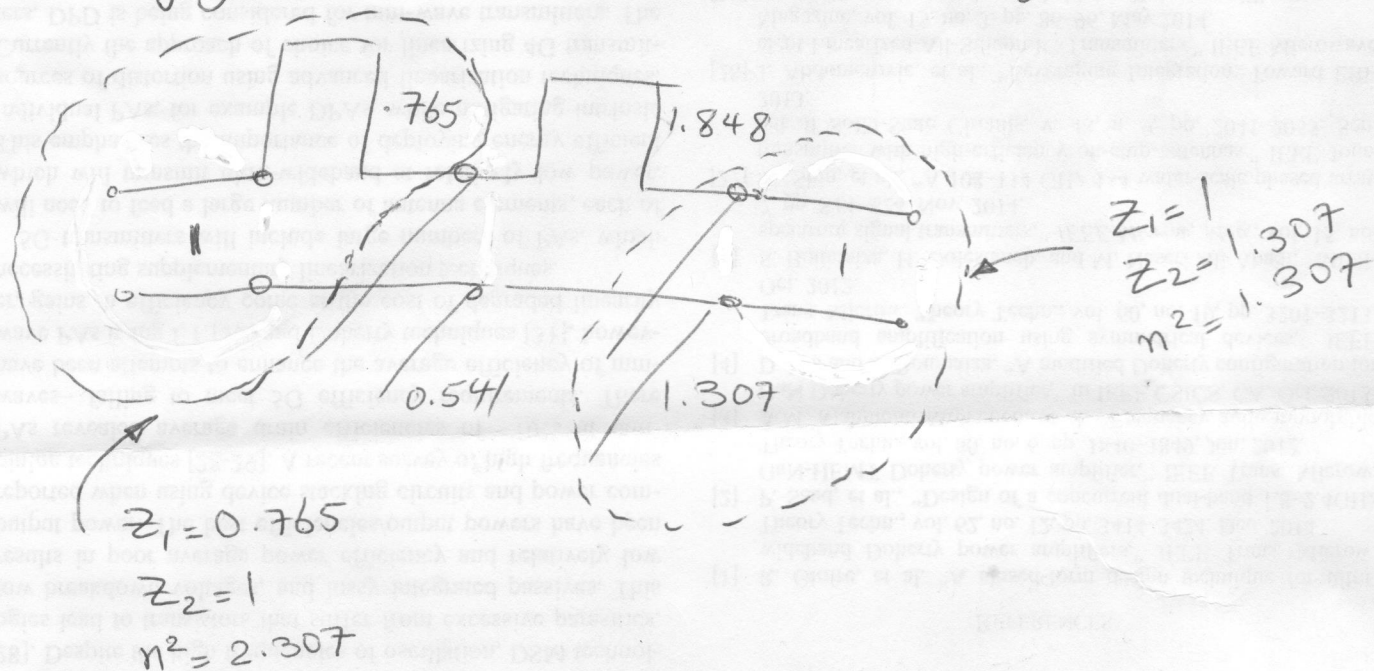


a) Applying Richard Transformation and add U.E.s




Use Kuroda identities:

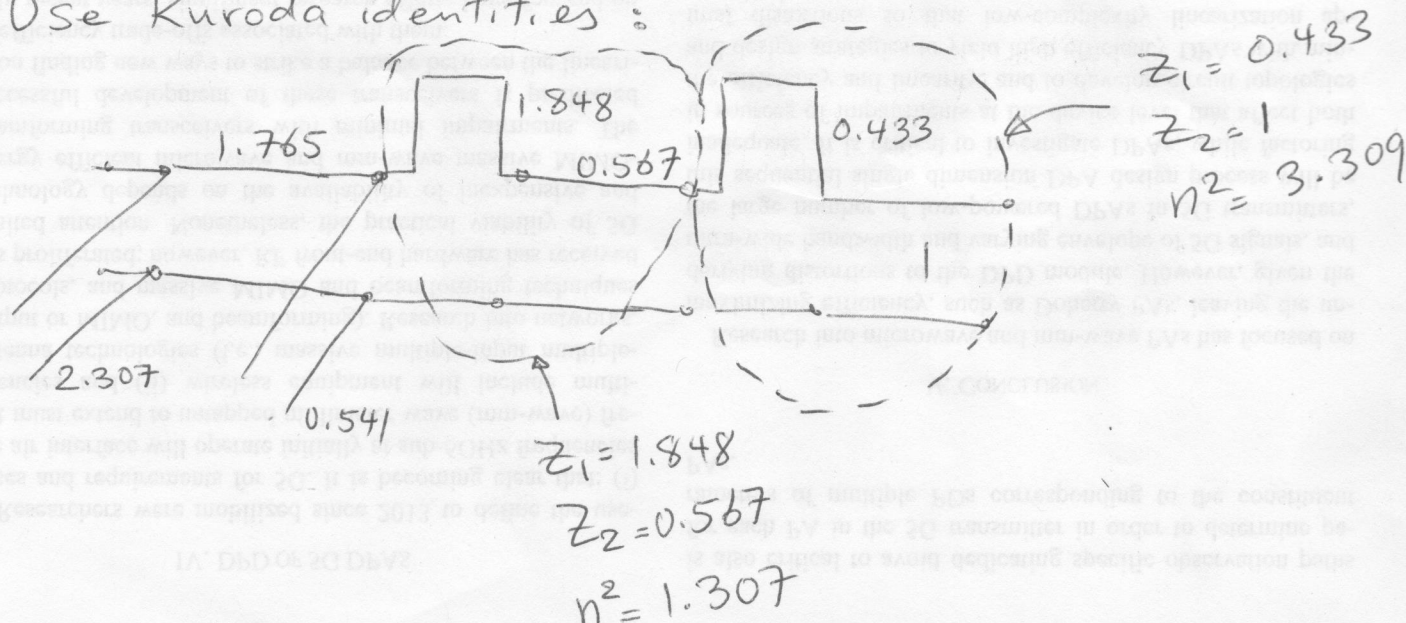

Q1) (Continue)

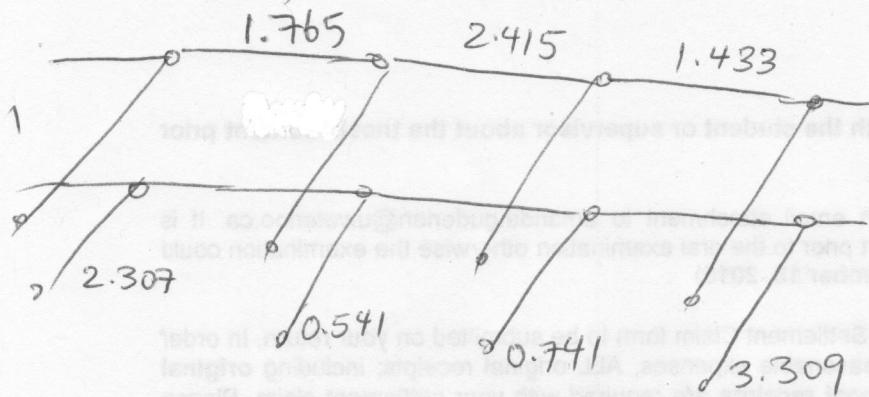

Scale to 50Ω :

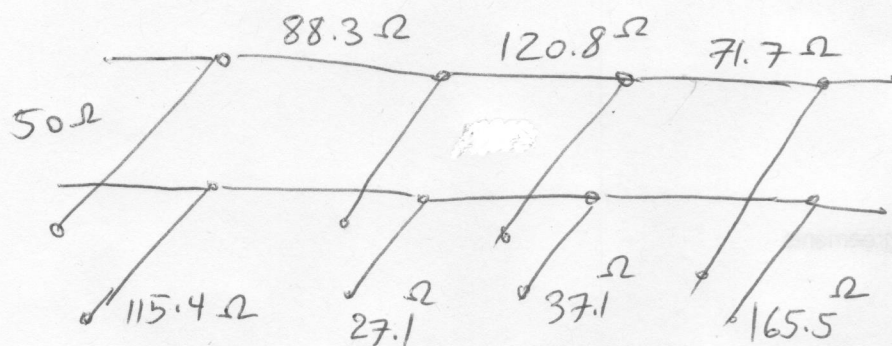

(all lines are $\lambda/8$ long @ 864 Hz)
 \downarrow
 $l \approx 135 \text{ mil}$

b) $Z_L = 10 \Omega$

$Z_h = 130 \Omega$

$\theta_L = \frac{L Z_0}{Z_h}$ (inductor)


$\theta_C = \frac{C Z_L}{Z_0}$ (capacitor)

$\left[\begin{array}{l} L, C \text{ are } \\ g_k \text{ values} \\ Z_0 = 50 \Omega \end{array} \right]$


Section	$Z_i (\Omega)$	$\theta_i (^\circ)$	$W_i (\text{mil})$	$L_i (\text{mil})$
1	130	16.9°	12	53
2	10	21.2°	692	60
3	130	40.7°	12	128
4	10	8.8°	692	25

blue: Ideal TLs, red: MLINs w/ discontinuities, magenta: original LC

(a)

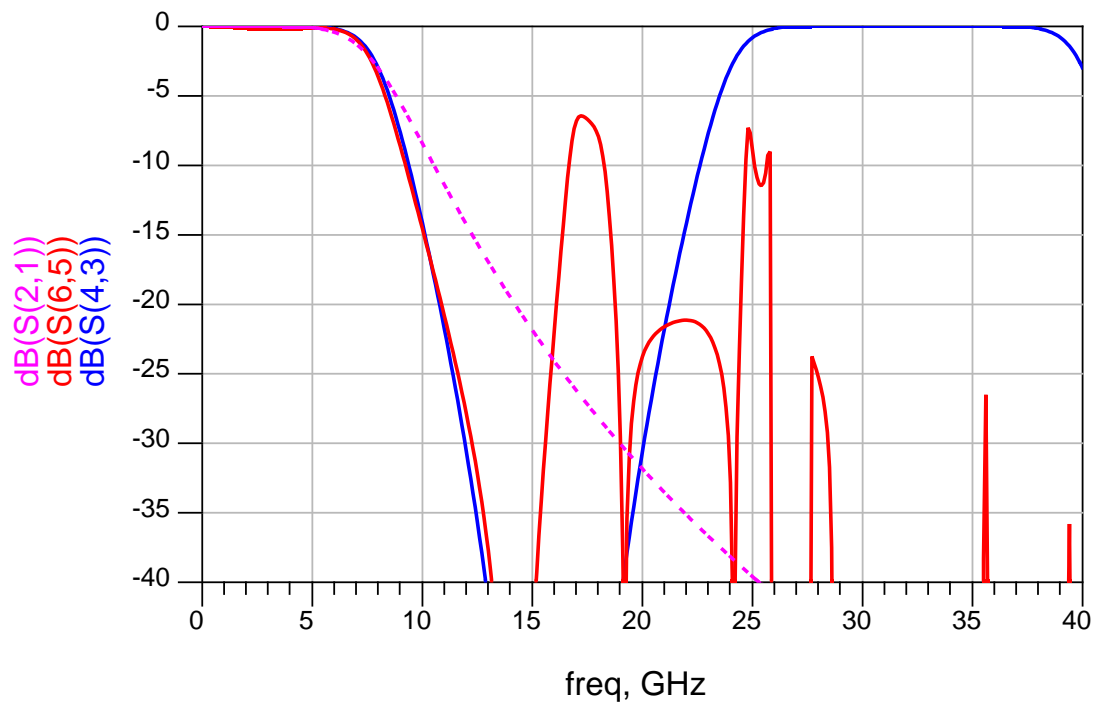

(b)

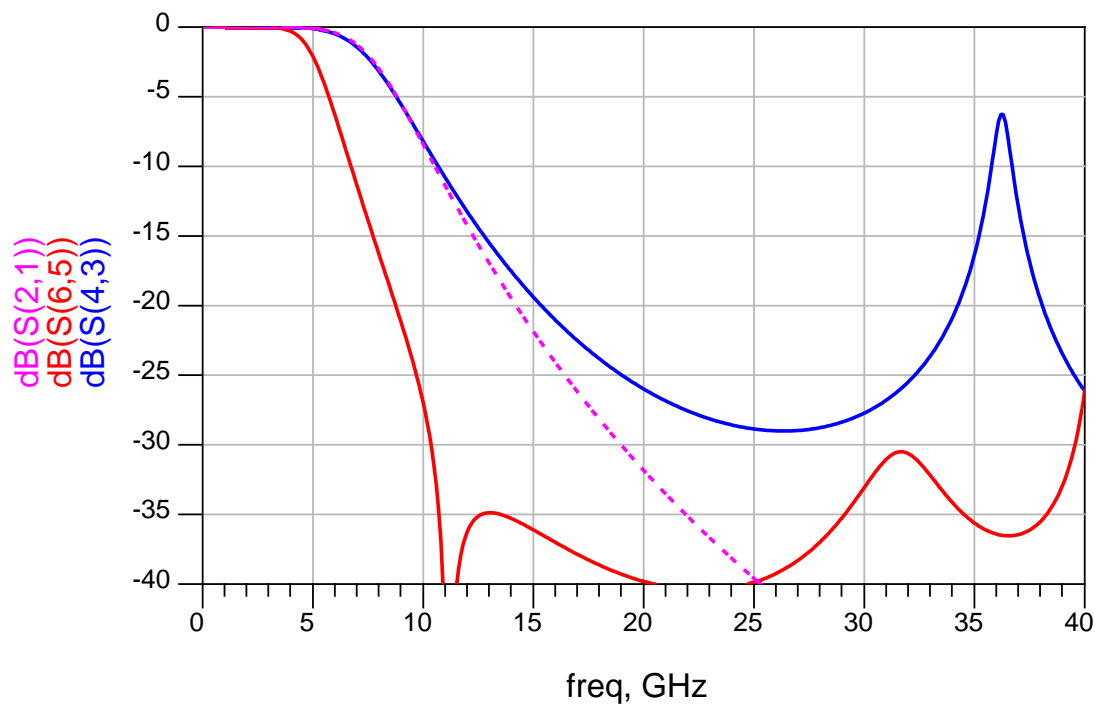

Q2. a)

$$f_0 = 3 \text{ GHz}, Z_0 = 75 \Omega, N = 3, \text{B.S.}, 0.5 \text{ dB E.R.}$$

First use (8.75) to transform 3.1 GHz to a L.P. prototype response frequency:


$$\omega \leftarrow \Delta \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1} = 0.1 \left(\frac{3.1}{3} - \frac{3}{3.1} \right)^{-1} = 1.52$$

So, $\left| \frac{\omega}{\omega_c} \right| - 1 = 0.52$, and Figure 8.27a gives an attenuation of 11 dB for $N = 3$. From Table 8.4, the prototype values are,

$$g_1 = 1.5963$$

$$g_2 = 1.0967$$

$$g_3 = 1.5963$$

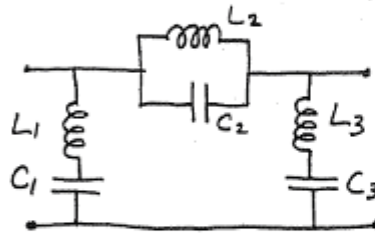

From Table 8.6 and (8.64) the scaled element values are,

$$L_1 = \frac{Z_0}{\omega_0 g_1 \Delta} = 24.9 \text{ nH} \quad \checkmark$$

$$C_1 = \frac{g_1 \Delta}{\omega_0 Z_0} = 0.113 \text{ pF} \quad \checkmark$$


$$L_2 = \frac{g_2 \Delta Z_0}{\omega_0} = 0.436 \text{ nH} \quad \checkmark$$

$$C_2 = \frac{1}{Z_0 \omega_0 g_2 \Delta} = 6.45 \text{ pF} \quad \checkmark$$

$$L_3 = \frac{Z_0}{\omega_0 g_3 \Delta} = 24.9 \text{ nH} \quad \checkmark$$

$$C_3 = \frac{g_3 \Delta}{Z_0 \omega_0} = 0.113 \text{ pF} \quad \checkmark$$

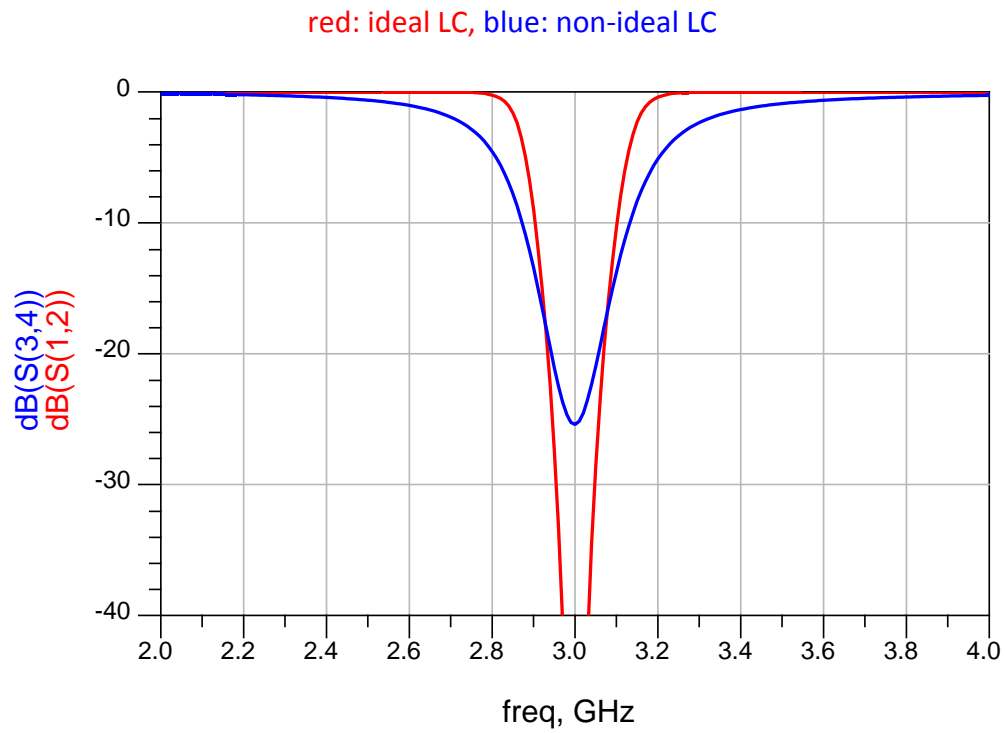The calculated response for this filter is shown on the following page. Note that the insertion loss at 3.1 GHz is about 10 dB.



Q3.

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix} \text{ for hybrid}$$

a) let $b = \lambda/4$ at $f_0 \Rightarrow \beta b = \pi/2$

Assume V_0^+ incident at T-junction. Then,

$$V_1^+ = V_0^+ e^{-j\beta(b-a)} = e^{-j\pi/2} e^{j\beta a}$$

$$V_4^+ = V_0^+ e^{-j\beta a}$$

$$V_2^- = \frac{-V_0^+}{\sqrt{2}} (jV_1^+ + V_4^+) = \frac{-V_0^+}{\sqrt{2}} (e^{j\beta a} + e^{-j\beta a}) = -\sqrt{2} V_0^+ \cos \beta a$$

$$P_2 = \frac{1}{2} |V_2^-|^2 = |V_0^+|^2 \cos^2 \beta a$$


$$V_3^- = \frac{-V_0^+}{\sqrt{2}} (V_1^+ + jV_4^+) = \frac{-V_0^+}{\sqrt{2}} (-je^{j\beta a} + je^{-j\beta a}) = -\sqrt{2} V_0^+ \sin \beta a$$

$$P_3 = \frac{1}{2} |V_3^-|^2 = |V_0^+|^2 \sin^2 \beta a$$

$$\text{So } \frac{P_3}{P_2} = \tan^2 \beta a = \tan^2 \frac{\pi a}{2b} \checkmark \quad (\text{since } \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{4b} = \frac{\pi}{2b})$$

b) For $\frac{P_3}{P_2} = 0.5$, $a = 0.098\lambda = 35.3^\circ$; $(b-a) = 0.152\lambda = 54.7^\circ$

CIRCUIT:

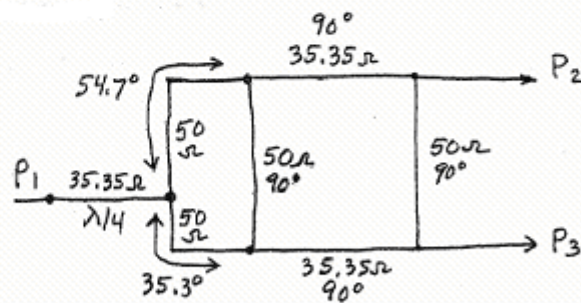

The S-parameters are plotted on the following page, for a center frequency of 1 GHz. Note that the power output ratios,

$$\frac{P_2}{P_1} = \frac{2}{3} = -1.76 \text{ dB} \quad \text{and} \quad \frac{P_3}{P_1} = \frac{1}{3} = -4.77 \text{ dB}$$


are verified.

03/06/04

Ansoft Corporation - Harmonica © SV 8.5

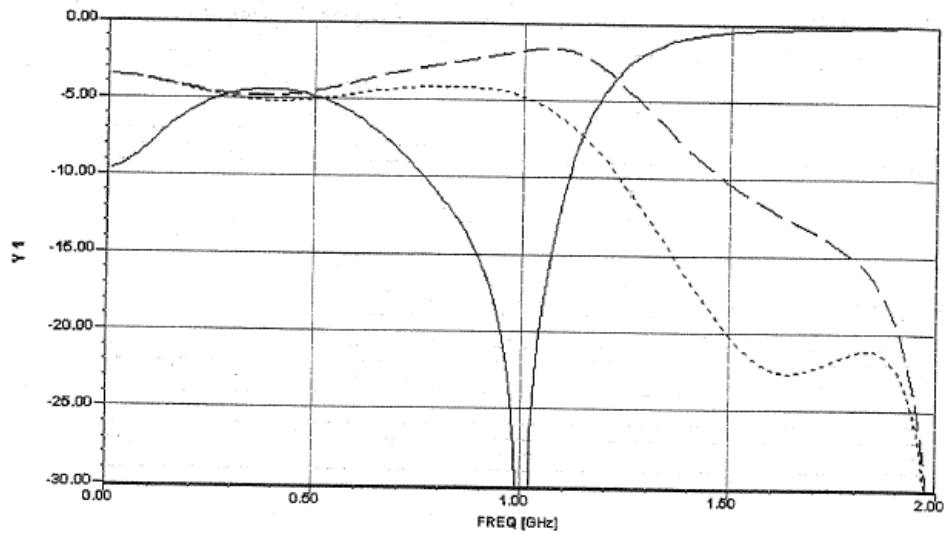17:00:45

C:\Documents and Settings\Administrator\Desktop\MEProblems\Pr7_33.olt



bailey Y1 dB(S11(dk=bailey))

bailey Y1 dB(S12(dk=bailey))

bailey Y1 dB(S13(dk=bailey))

Q4. First, note that $[S]_{coupler} = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$

a)

$$RF_7 = S_{42}RF_3 + S_{43}RF_5 = \frac{j}{\sqrt{2}}(RF_3 - RF_5)$$

$$\frac{RF_2}{RF_1} = 0.93 \equiv -0.63 \text{ dB}, \quad \frac{RF_5}{RF_2} = 0.03 \equiv -30.46 \text{ dB}$$

Hence,

$$\frac{RF_5}{RF_1} = 0.93 \times 0.03 = 0.0279 = -31.09 \text{ dB}$$

Also,

$$\frac{RF_3}{RF_1} = S_{13}^{CRLTR} \cdot S_{12}^{CRLTR} = 0.03 \times 0.93 = 0.0279 = -31.09 \text{ dB}$$

$$\frac{RF_7}{RF_1} = \frac{j}{\sqrt{2}} \left(\frac{RF_3}{RF_1} - \frac{RF_5}{RF_1} \right) = 0$$

b) We have built an ideal circulator using non-ideal circulators and a 180° hybrid coupler