

```

In[581]:= Δ[S11_, S12_, S21_, S22_] := S11 S22 - S12 S21;

K[S11_, S12_, S21_, S22_] := 
$$\frac{1 - \text{Abs}[S11]^2 - \text{Abs}[S22]^2 + \text{Abs}[\Delta[S11, S12, S21, S22]]^2}{2 \text{Abs}[S12 S21]}$$


Phase[S_] := Exp[I S Pi / 180];

B1[S11_, S12_, S21_, S22_] := 1 + Abs[S11]^2 - Abs[S22]^2 - Abs[Δ[S11, S12, S21, S22]]^2;
B2[S11_, S12_, S21_, S22_] := 1 - Abs[S11]^2 + Abs[S22]^2 - Abs[Δ[S11, S12, S21, S22]]^2;
C1[S11_, S12_, S21_, S22_] := S11 - Δ[S11, S12, S21, S22] Conjugate[S22];
C2[S11_, S12_, S21_, S22_] := S22 - Δ[S11, S12, S21, S22] Conjugate[S11];

Γpms[S11_, S12_, S21_, S22_] := (B1[S11, S12, S21, S22] + Sqrt[B1[S11, S12, S21, S22]^2 - 4 Abs[C1[S11, S12, S21, S22]]^2]) / (2 C1[S11, S12, S21, S22]);
Γmms[S11_, S12_, S21_, S22_] := (B1[S11, S12, S21, S22] - Sqrt[B1[S11, S12, S21, S22]^2 - 4 Abs[C1[S11, S12, S21, S22]]^2]) / (2 C1[S11, S12, S21, S22]);
Γpm1[S11_, S12_, S21_, S22_] := (B2[S11, S12, S21, S22] + Sqrt[B2[S11, S12, S21, S22]^2 - 4 Abs[C2[S11, S12, S21, S22]]^2]) / (2 C2[S11, S12, S21, S22]);
Γmm1[S11_, S12_, S21_, S22_] := (B2[S11, S12, S21, S22] - Sqrt[B2[S11, S12, S21, S22]^2 - 4 Abs[C2[S11, S12, S21, S22]]^2]) / (2 C2[S11, S12, S21, S22]);

GTMax1[S11_, S12_, S21_, S22_, Γ1_, Γs_] :=
  ((1 - Abs[Γs]^2) Abs[S21]^2 (1 - Abs[Γ1]^2)) / Abs[(1 - S11 Γs) (1 - S22 Γ1) - S12 S21 Γs Γ1]^2

GTMax2[S12_, S21_, K_] := 
$$\frac{\text{Abs}[S21]}{\text{Abs}[S12]} (K - \text{Sqrt}[K^2 - 1]);$$


```

```

In[592]:= (* Below are the scattering parameters at 2GHz obtained with the
           physical bias network. I have added a shunt resistor to the gate to
           make the transistor unconditionally stable at the design frequency. *)

```

```

In[593]:= S11 = .006 Phase[-120.590];
           S12 = .006 Phase[-120.707];
           S21 = .530 Phase[-95.725];
           S22 = .996 Phase[178.086];

```

```

In[597]:= Abs[Δ[S11, S12, S21, S22]]

```

```

Out[597]= 0.0065743

```

```

In[598]:= K1 = K[S11, S12, S21, S22]

```

```

Out[598]= 1.25648

```

```
In[599]:= Abs[(ΓP)m1[S11, S12, S21, S22]];
```

```
Γm1 = (Γm)m1[S11, S12, S21, S22]
```

```
Abs[(ΓP)ms[S11, S12, S21, S22]];
```

```
Γms = (Γm)ms[S11, S12, S21, S22]
```

```
Out[600]= -0.997018 - 0.0332993 i
```

```
Out[602]= 0.403474 + 0.286539 i
```

```
In[603]:= Gtmax1 = 10 Log10[GTMax1[S11, S12, S21, S22, Γm1, Γms]]
```

```
Gtmax2 = 10 Log10[GTMax2[S12, S21, K1]]
```

```
Out[603]= 16.4137
```

```
Out[604]= 16.4137
```

```
(* Below begins the analytical calculations
for the matching network of the device. *)
```

```
In[606]:= Abs[Γm1] && Arg[Γm1] * 180 / Pi
```

```
Out[606]= 0.997574 && -178.087
```

```
In[607]:= Abs[Γms] && Arg[Γms] * 180 / Pi
```

```
Out[607]= 0.49487 && 35.3816
```

```
In[608]:= Γms = .529 Phase[35.336];
```

```
In[609]:= Zm1 = 50 *  $\frac{1 + \Gamma_{m1}}{1 - \Gamma_{m1}}$ ;
```

```
In[610]:= Zms = 50 *  $\frac{1 + \Gamma_{ms}}{1 - \Gamma_{ms}}$ ;
```

```
In[611]:= Ym1 = 1 / Zm1;
```

```
In[612]:= Lengths[l1_, ls_] := Yc  $\frac{(1 + i \tan[l1] + i \tan[ls])}{1 + i \tan[l1] - \tan[ls] \tan[l1]}$ ;
```

```
Yc = 1 / 50;
```

```
In[614]:= {x, y} = {l1, ls} /. FindRoot[
  {Re[Lengths[l1, ls]] == Re[Ym1], Im[Lengths[l1, ls]] == Im[Ym1]}, {l1, .2}, {ls, .6}]
{x,
 y} *
 180 /
 Pi
```

```
Out[614]= {0.0181423, 1.53592}
```

```
Out[615]= {1.03948, 88.0016}
```

(* The above tells me that the load matching network should comprise a series stub that is ~1.04 degrees long (I can add 180 degrees with no penalty) and an open stub that is ~88 degrees long. *)

In[617]:= $Y_{ms} = \frac{1}{Z_{ms}};$

{x, y} = {l1, ls} /. FindRoot[
 {Re[Lengths[l1, ls]] == Re[Yms], Im[Lengths[l1, ls]] == Im[Yms]}, {l1, .7}, {ls, .7}]

Out[618]= {1.76912, 0.894776}

In[619]:= {x, y} * 180 / Pi

Out[619]= {101.363, 51.2669}

In[620]:=

(* The above tells me that the source matching network should comprise a series stub that is ~101.4 degrees long and a shunt open stub that is ~51.3 degrees long. *)