

Q1) a) $P_{avs} = \frac{|V_s|^2}{8R_s} = \frac{20^2}{8 \times 100} = 0.5 \text{ W}$

$V_s = 20 \angle 0^\circ \text{ V}$

$R_s = 100 \Omega$

$Z_0 = 50 \Omega$

$R_L = 50 \Omega$

b) $b_1 = S_{11} a_1 + S_{12} a_2$

$b_2 = S_{21} a_1 + S_{22} a_2$

$\frac{a_2}{b_2} = \Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = 0 \rightarrow a_2 = 0$

$V_1 = \frac{Z_{in}}{R_s + Z_{in}} V_s = V_1^+ + V_1^- = \sqrt{Z_0} (a_1 + b_1) = \sqrt{Z_0} a_1 (1 + \Gamma_{in})$

$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = S_{11}$ (Port 2 is matched) \textcircled{I}

$\textcircled{I} \textcircled{II} \Rightarrow a_1 = \frac{V_s}{2\sqrt{Z_0}} \frac{Z_{in} + Z_0}{Z_{in} + R_s}, \quad Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}$

Substitution $\rightarrow a_1 = 0.9705 - j0.0167 = 0.971 \angle -1^\circ$
 $b_1 = S_{11} a_1 = 0.0832 - j0.05 = 0.097 \angle -31^\circ$
 $b_2 = S_{21} a_1 = 0.6408 - j0.6632 = 0.922 \angle -46^\circ$

Q1] c) Wrong: $P_{\text{ref}} = \frac{|b_1|^2}{2} = 0.0047 \text{ W}$

because a_1, b_1 are referenced to $50\text{-}\Omega$
whereas $R_s = 100\text{-}\Omega$

Correct: $\Gamma_{\text{in}}' = \frac{Z_{\text{in}} - R_s}{Z_{\text{in}} + R_s} = 0.26 \angle -169.5^\circ$

$P_{\text{ref}} = P_{\text{avs}} |\Gamma_{\text{in}}'|^2 = 33.6 \text{ mW} = 0.0336 \text{ W}$

$P_{\text{del}} = \frac{|b_2|^2 - |a_2|^2}{2} = 0.4252 \text{ W}$

- An alternative approach is to write $[b] = [S][a]$ in $100\text{-}\Omega$ system. For that, you need to convert the $[S]$ ~~to~~ from $50\text{-}\Omega$ to $100\text{-}\Omega$, a_i 's and b_i 's in that case would be referenced to $100\text{-}\Omega$.
- Even though in this case $P_{\text{ref}} \neq \frac{|b_1|^2}{2}$ (as mentioned above), the equations for power delivered are still valid, so

$P_{\text{in}} = \frac{|b_1|^2 - |a_1|^2}{2} = P_{\text{avs}} - P_{\text{ref}} = 0.466 \text{ W}$

Power delivered to the 2PN

~~A portion of this power is reflected at the load~~


Q2.

For single OC shunt stub matching:

$$d_1 = 0.348\lambda, l_1 = 0.098\lambda, \text{ or } d_2 = 0.152\lambda, l_2 = 0.402\lambda$$

For lumped LC matching:

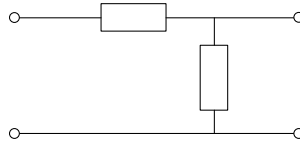
$$L_s = 7.96 \text{ nH}, C_p = 1.59 \text{ pF}, \text{ or } C_s = 3.18 \text{ pF}, L_p = 15.9 \text{ nH}$$



For double OC shunt stub matching with $d = \lambda/8$:

$$l_1 = 0.194\lambda, l_2 = 0.172\lambda, \text{ or } l_1 = 0.399\lambda, l_2 = 0.021\lambda$$

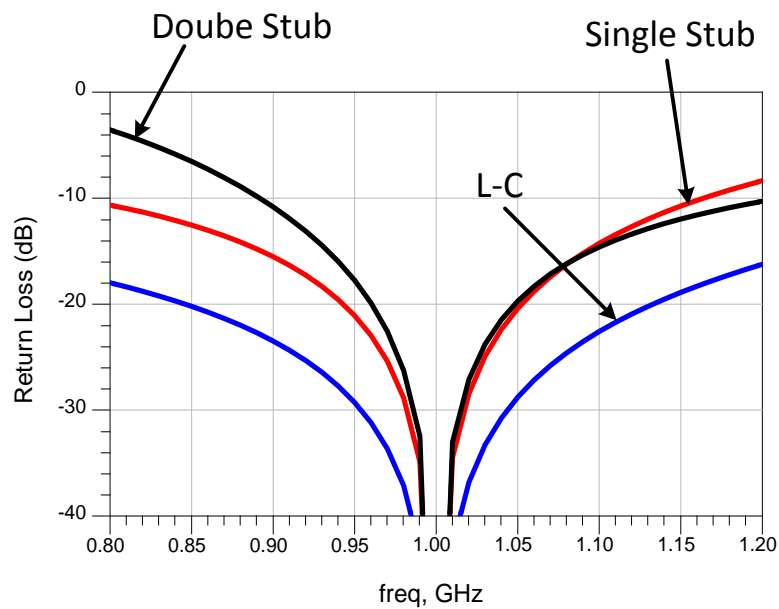According to the Figure below, LC-matching has the best bandwidth.



Q3

Using 5.3(a) & (b):

($R_L/R_S = N^2$,
 $X_L = 0, Z_0 = R_S$)

$$\omega_0 C = B = \frac{N \sqrt{R_L^2 - R_L R_S}}{R_L^2}$$



$$\omega_0 C = \frac{N}{R_L^2} \cdot R_L \sqrt{1 - \frac{1}{N^2}}$$

$$C = \frac{N}{\omega_0 R_L} \cdot \frac{\sqrt{N^2 - 1}}{N} = \frac{\sqrt{N^2 - 1}}{R_L \omega_0} \quad \textcircled{I}$$

$$\omega_0 L = X = \frac{R_L}{\sqrt{N^2 - 1}} \cdot \left(1 - \frac{R_S}{R_L}\right)$$

$$\omega_0 L = \frac{R_L}{\sqrt{N^2 - 1}} \left(\frac{N^2 - 1}{N^2}\right) = R_S \sqrt{N^2 - 1}$$
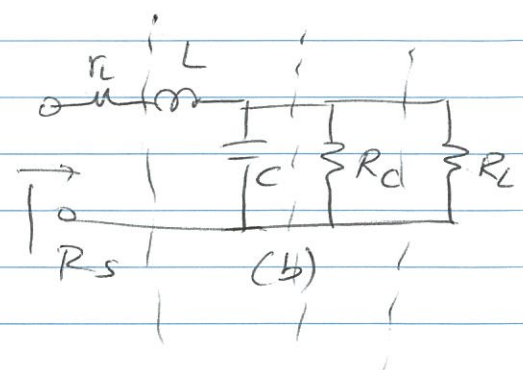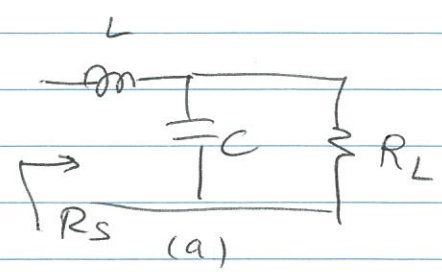
$$\Rightarrow L = \frac{R_S \sqrt{N^2 - 1}}{\omega_0} \quad \textcircled{II}$$



$$I.L = \frac{P_L}{P_{in}} = \frac{P_L}{P'_L} \cdot \frac{P'_L}{P'_{in}} \cdot \frac{P'_{in}}{P_{in}}$$

$$\approx \frac{R_C \parallel R_L}{R_L} \cdot 1 \cdot \frac{R_S}{R_L + R_S}$$

$$= \frac{R_C}{R_L + R_C} \cdot \frac{R_S}{R_L + R_S}, \quad \begin{cases} Q_C = R_C \cdot C \omega_0 \\ Q_L = \frac{\omega_0 L}{R_L} \end{cases}$$

$$R_C = \frac{Q_C}{\omega_0 C}, \quad r_L = \frac{\omega_0 L}{Q_L}$$

Assuming $Q \gg 1$

Note that if $\begin{cases} R_C \rightarrow \infty \\ r_L \rightarrow 0 \end{cases}$ then $I.L = 1 \equiv 0 \text{ dB}$

T

$$I.L = \frac{1}{1 + R_L/R_0} \cdot \frac{1}{1 + r_L/R_S}$$

$$IL = \frac{1}{1 + \frac{R_L \omega C}{Q_C}} \cdot \frac{1}{1 + \frac{\omega L}{R_S Q_L}}$$

$$IL = \frac{1}{1 + \frac{R_L}{Q_C} \frac{\sqrt{N^2-1}}{R_L}} \cdot \frac{1}{1 + \frac{1}{R_S Q_L} R_S \sqrt{N^2-1}} = \frac{1}{1 + \frac{\sqrt{N^2-1}}{Q_C}} \cdot \frac{1}{1 + \frac{\sqrt{N^2-1}}{Q_L}} \quad \text{III}$$

In this example: $Q_C = 30$
 $Q_L = 15$
 $R_L/R_S = N^2 = 5$

\Rightarrow Using III: $IL = 0.8272$
 $= +0.82 \text{ dB}$

From ADS Simulation: $I.L. = +0.835 \text{ dB}$

\therefore Hand Analysis is in very good agreement with simulation

Q4

$$b_2 = S_{22} a_2 + S_{23} a_3 \quad \textcircled{I}$$

$$a_3 = b_4 e^{-j\pi/4} \quad \textcircled{II}$$

$$b_4 = S_{41} a_1 + S_{44} a_4 \quad \textcircled{III}$$

$$a_4 = b_3 e^{-j\pi/4} \quad \textcircled{IV}$$

$$b_3 = S_{32} a_2 + S_{33} a_3 \quad \textcircled{V}$$

$$\begin{aligned} \textcircled{II} \Rightarrow a_3 &= e^{-j\pi/4} (S_{41} a_1 + S_{44} a_4) \\ &= e^{-j\pi/4} (S_{41} a_1 + S_{44} b_3 e^{-j\pi/4}) \end{aligned}$$

$$\Rightarrow a_3 = e^{-j\pi/4} (S_{41} a_1 + S_{44} S_{33} e^{-j\pi/4} a_3)$$

$$\Rightarrow a_3 = \frac{e^{-j\pi/4} S_{41}}{1 - j S_{44} S_{33}} a_1 \quad \textcircled{VI}$$


$$\textcircled{I, VI} \Rightarrow \frac{b_2}{a_1} = \frac{e^{-j\pi/4} S_{41} S_{23}}{1 + j S_{44} S_{33}}$$

Substitution $\rightarrow \frac{b_2}{a_1} = 0.4 \angle -135^\circ$


$\rightarrow IL = -7.96 \text{ dB}$

$\rightarrow \text{delay} = 135^\circ$

Q5

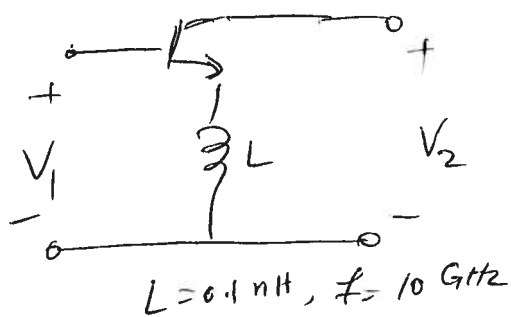

\equiv

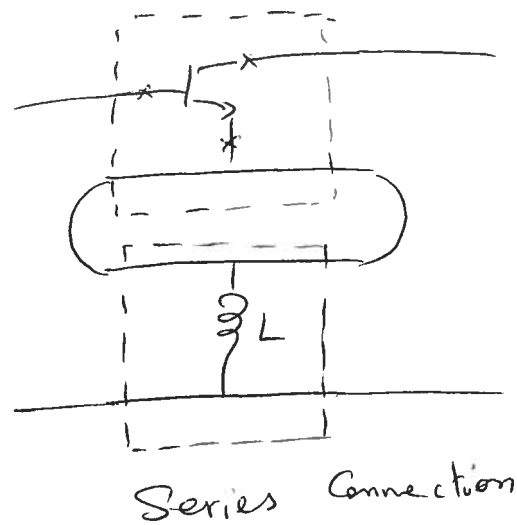

$$Z_T = Z_{tr} + Z_L$$

$$Z_L = \begin{bmatrix} j\omega L & j\omega L \\ j\omega L & j\omega L \end{bmatrix} = \begin{bmatrix} j6.28 & j6.28 \\ j6.28 & j6.28 \end{bmatrix}$$

$$[S]_{tr} \rightarrow [Z]_{tr} = \begin{bmatrix} 26.56 \angle -68.42^\circ & 0 \\ 139.958 \angle -143.128^\circ & 98.62 \angle -69.68^\circ \end{bmatrix}$$


$$[Z_T] = [Z]_{tr} + [Z]_L$$

$$\therefore [Z_T] = \begin{bmatrix} 20.84 \angle -62.06^\circ & 6.28 \angle 90^\circ \\ 136.28 \angle -145.24^\circ & 92.7 \angle -68^\circ \end{bmatrix}$$

$$(Z_0 = 50 \Omega)$$

$$[S]_T = \begin{bmatrix} 0.9064 \angle -141.9^\circ & 0.0944 \angle 153.7^\circ \\ 2.0374 \angle -81.5^\circ & 0.7684 \angle -62.2^\circ \end{bmatrix}$$

Q6

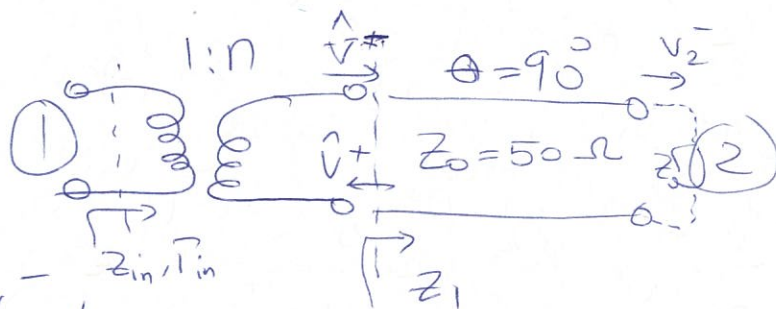

$$(1) S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \Gamma_{in} \Big|_{\text{Port 2 is matched}} = ?$$

$$Z_1 = \frac{Z_0}{n^2} \rightarrow Z_{in} = \frac{Z_0}{n^2} \Rightarrow \Gamma_{in} = \frac{\frac{Z_0}{n^2} - Z_0}{\frac{Z_0}{n^2} + Z_0}$$

$$\therefore S_{11} = \frac{1 - n^2}{1 + n^2}$$

$$(2) S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} = ?$$


$$V_2^- = \hat{V}^- e^{-j\pi/2} \quad (I)$$

$$\begin{cases} \hat{V}^- = V_1^+ n \Rightarrow \hat{V}^+ + \hat{V}^- = (V_1^+ + V_1^-) n \\ \hat{V}^+ = V_2^+ e^{-j\pi/2} = 0 \end{cases}$$

$$\Rightarrow \hat{V}^- = V_1^+ (1 + S_{11}) n \quad (II)$$

$$(I, II) \Rightarrow S_{21} = -jn^2(1 + S_{11}) = -j \frac{2n}{1 + n^2} = S_{12}$$

Q6) (3) $S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{V_1^+ = 0} = \left. \Gamma_{out} \right|_{\text{Port 1 matched}} = ?$

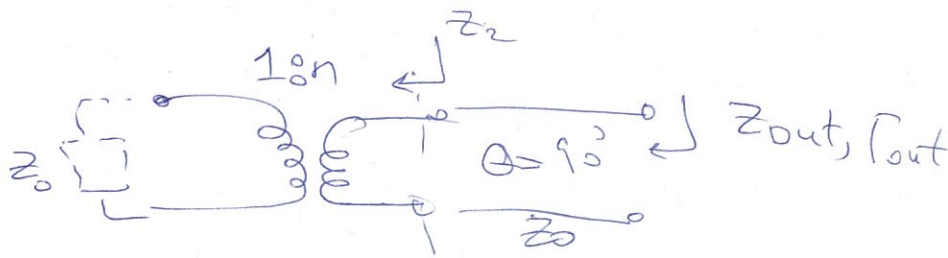

$$Z_2 = n^2 Z_0, Z_{out} = \frac{Z_0^2}{Z_2} = \frac{Z_0}{n^2} = Z_{in}$$

$$\Rightarrow S_{22} = \frac{1 - n^2}{1 + n^2}$$