
Values used everywhere

```
In[60]:= S11 = .1 Exp[-I 30 °];  
S12 = .4 Exp[-I 75 °];  
S21 = .95 Exp[-I 45 °];  
S22 = .15 Exp[-I 10 °];  
Vs = 20 V;  
Zs = 100 Ω;  
Zc = 50 Ω;  
Z1 = 50 Ω;
```

Attempt at a reference-impedance-free solution:

```
In[63]:= Gammas =  
FullSimplify[Solve[{Γins == S11 -  $\frac{S12 S21 \Gamma_{outs}}{1 + S22 \Gamma_{outs}}$ , Γouts == S22 -  $\frac{S12 S21 \Gamma_{ins}}{1 + S11 \Gamma_{ins}}$ }, {Γins, Γouts}]];  
{Γin1, Γout1} = ({Γins, Γouts} /. Gammas)[[1]]  
{Γin2, Γout2} = ({Γins, Γouts} /. Gammas)[[2]]  
Zin = Zs  $\frac{1 + \Gamma_{in2}}{1 - \Gamma_{in2}}$   
Γin = Γin2  
Γ1 = -Γout2
```

Solve::ratnz : Solve was unable to solve the system with inexact coefficients.

The answer was obtained by solving a corresponding exact system and numericizing the result. >>

```
Out[64]= {-8.78584 + 0.458246 i, -5.95836 + 0.433468 i}
```

```
Out[65]= {0.113511 + 0.00592043 i, 0.166948 + 0.0121454 i}
```

```
Out[66]= (125.599 + 1.50666 i) Ω
```

```
Out[67]= 0.113511 + 0.00592043 i
```

```
Out[68]= -0.166948 - 0.0121454 i
```

```
In[69]:= a1 =  $\frac{V_s}{2 \sqrt{Z_c}}$ 
```

```
Out[69]=  $\sqrt{2} \text{ V} / \sqrt{\Omega}$ 
```

$$\text{In[70]:= } \mathbf{b_1} = \frac{\mathbf{V_s}}{2 \sqrt{\mathbf{Z_c}}} \Gamma_{\text{in}}$$

$$\text{Out[70]= } (0.160528 + 0.00837275 i) V / \sqrt{\Omega}$$

$$\text{In[71]:= } \mathbf{a_2} = \frac{\mathbf{V_s}}{2 \sqrt{\mathbf{Z_c}}} \frac{\mathbf{S_{21}} \Gamma_L}{1 - \mathbf{S_{22}} \Gamma_L}$$

$$\text{Out[71]= } \frac{\left((0.95 - 0.95 i) V / \sqrt{\Omega} \right) \Gamma_L}{1 - (0.147721 - 0.0260472 i) \Gamma_L}$$

$$\text{In[72]:= } \mathbf{b_2} = \frac{\mathbf{V_s}}{2 \sqrt{\mathbf{Z_c}}} \frac{\mathbf{S_{21}}}{1 - \mathbf{S_{22}} \Gamma_L}$$

$$\text{Out[72]= } \frac{(0.95 - 0.95 i) V / \sqrt{\Omega}}{1 - (0.147721 - 0.0260472 i) \Gamma_L}$$

$$\text{In[73]:= } \mathbf{P_{load}} = \text{UnitConvert} \left[\frac{1}{2} \text{Re} \left[\sqrt{\mathbf{Z_c}} (\mathbf{a_2} + \mathbf{b_2}) \text{Conjugate} \left[\frac{\sqrt{\mathbf{Z_c}} (\mathbf{a_2} + \mathbf{b_2})}{\mathbf{Z_L}} \right] \right], \text{"milliWatts"} \right]$$

Thread::tdlen :

Objects of unequal length in {{0.852279 - 0.0260472 i, 1 + Conjugate[Γ_L]}, Quantity[0.95 + 0.95 i, {Ohms, Volts}]} + {{0.852279 - 0.0260472 i, 1 + Conjugate[Γ_L]}, Conjugate[Γ_L], Quantity[0.95 + 0.95 i, {Ohms, Volts}]} cannot be combined. >>

Thread::tdlen : Objects of unequal length in

{Quantity[0.95 - 0.95 i, {Ohms, Volts}], {0.852279 + 0.0260472 i, 1 + Γ_L}} + {Quantity[0.95 - 0.95 i, {Ohms, Volts}], {0.852279 + 0.0260472 i, 1 + Γ_L}, Γ_L} cannot be combined. >>

Thread::tdlen : Objects of unequal length in

{{0.852279, 1 + Re[Γ_L]}, Re[Quantity[0.95 + 0.95 i, {Ohms, Volts}]]} + {{0.852279, 1 + Re[Γ_L]}, Re[Γ_L], Re[Quantity[0.95 + 0.95 i, {Ohms, Volts}]]} cannot be combined. >>

General::stop : Further output of Thread::tdlen will be suppressed during this calculation. >>

$$\begin{aligned} \text{Out[73]= } & \text{UnitConvert} \left[\frac{1}{2} \text{Re} \left[\frac{1}{\text{Conjugate}[Z_L]} \left(\frac{(0.95 + 0.95 i) V / \sqrt{\Omega}}{1 - (0.147721 + 0.0260472 i) \text{Conjugate}[\Gamma_L]} + \right. \right. \right. \\ & \left. \left. \frac{\text{Conjugate}[\Gamma_L] \left((0.95 + 0.95 i) V / \sqrt{\Omega} \right)}{1 - (0.147721 + 0.0260472 i) \text{Conjugate}[\Gamma_L]} \right) \right] (50 \Omega) \\ & \left. \left(\frac{(0.95 - 0.95 i) V / \sqrt{\Omega}}{1 - (0.147721 - 0.0260472 i) \Gamma_L} + \frac{\left((0.95 - 0.95 i) V / \sqrt{\Omega} \right) \Gamma_L}{1 - (0.147721 - 0.0260472 i) \Gamma_L} \right) \right], \text{milliWatts}] \end{aligned}$$

$$\text{In[74]:= } P_{\text{ref}} = \text{UnitConvert}\left[\frac{1}{2} \frac{\text{Abs}[V_s]^2}{\text{Abs}[Z_s + Z_{\text{in}}]^2} \text{Re}[Z_s], \text{"milliWatts"}\right]$$

$$\text{Out[74]= } 392.949 \text{ mW}$$

$$\text{In[75]:= } P_{\text{used}} = \text{UnitConvert}\left[\frac{1}{2} \text{Re}\left[V_s \text{Conjugate}\left[\frac{(a_1 + b_1)}{Z_{\text{in}}} \text{Sqrt}[Z_c]\right]\right], \text{"milliWatts"}\right]$$

$$\text{Out[75]= } 886.489 \text{ mW}$$

$$\text{In[76]:= } P_{\text{network}} = \text{UnitConvert}\left[\frac{1}{2} \text{Re}\left[V_s \frac{Z_{\text{in}}}{Z_{\text{in}} + Z_s}\right] \text{Conjugate}\left[\frac{V_s}{Z_{\text{in}} + Z_s}\right]\right], \text{"milliWatts"}\right]$$

$$\text{Out[76]= } 493.54 \text{ mW}$$

$$\text{In[77]:= } P_{\text{network}} + P_{\text{ref}}$$

$$\text{Out[77]= } 886.489 \text{ mW}$$

$$\text{In[78]:=}$$

Reference Impedance Solution

$$\text{Out[78]= } \text{Reference Impedance Solution}$$

$$\text{In[79]:= } Z_{c_1} = 100 \, \Omega ; Z_{c_2} = 50 \, \Omega ; \Gamma_1 = \frac{Z_1 - Z_{c_2}}{Z_1 + Z_{c_2}} ; \Gamma_{\text{in}} = S_{11} + \frac{S_{12} S_{21} \Gamma_1}{1 - S_{22} \Gamma_1} ; \Gamma_s = \frac{Z_s - Z_{c_1}}{Z_s + Z_{c_1}} ;$$

$$Z_{\text{in}} = Z_{c_1} \frac{(1 + \Gamma_{\text{in}})}{1 - \Gamma_{\text{in}}} ;$$

$$a_1 = \text{UnitConvert}\left[N\left[\frac{V_s}{\sqrt{Z_{c_1}}} \frac{Z_{\text{in}}}{Z_s + Z_{\text{in}}} \frac{1}{1 + \Gamma_{\text{in}}}\right], \text{"SI"}\right]$$

$$\text{Out[81]= } (1. + 1.38778 \times 10^{-17} i) \text{ V}/\sqrt{\Omega}$$

$$\text{In[82]:= } b_1 = \Gamma_{\text{in}} a_1$$

$$\text{Out[82]= } (0.0866025 - 0.05 i) \text{ V}/\sqrt{\Omega}$$

$$\text{In[83]:= } b_2 = a_1 \frac{S_{21}}{1 - \Gamma_1 S_{22}}$$

$$\text{Out[83]= } (0.671751 - 0.671751 i) \text{ V}/\sqrt{\Omega}$$

$$\text{In[84]:= } a_2 = b_2 \Gamma_1$$

$$\text{Out[84]= } (0. + 0. i) \text{ V}/\sqrt{\Omega}$$

```
In[85]:= Pload = UnitConvert[ $\frac{1}{2} \operatorname{Re}\left[\sqrt{Z_{c_2}} (a_2 + b_2) \operatorname{Conjugate}\left[\sqrt{Z_{c_2}} \frac{a_2 + b_2}{Z_1}\right]\right]$ , "milliWatts"]
```

```
Out[85]= 451.25 mW
```

```
In[86]:= Psource = UnitConvert[ $\frac{1}{2} \operatorname{Re}\left[\left(V_s \frac{Z_s}{Z_{in} + Z_s}\right) \operatorname{Conjugate}\left[\frac{V_s}{Z_{in} + Z_s}\right]\right]$ , "milliWatts"]
```

```
Out[86]= 418.397 mW
```

```
In[87]:= Pnetwork = UnitConvert[ $\frac{1}{2} \operatorname{Re}\left[(a_1 + b_1) \operatorname{Conjugate}[a_1 - b_1]\right]$ , "milliWatts"]
```

```
Out[87]= 495. mW
```

```
In[89]:= Pdel = UnitConvert[ $\frac{1}{2} \operatorname{Re}\left[\frac{V_s^2}{\operatorname{Conjugate}[Z_{in} + Z_s]}\right]$ , "milliWatts"]
```

```
Out[89]= 913.397 mW
```

```
In[90]:= Pnetwork + Psource
```

```
Out[90]= 913.397 mW
```